

CONTINUOUS INTERNAL EVALUATION - 3

Dept:EC	Sem / Div:1 st D, E, F	Sub: Basic Electronics	S Code: 18ELN14
Date:09/04/21	Time: 9:30-11:00AM	Max Marks: 50	Elective:N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
PART A				
1	a Explain the voltage series feedback circuit and derive an equation for voltage gain A_v with feedback.	7	L2	CO1
	b Explain the basic elements of communication system with block diagram.	7	L2	CO5
	c State and prove De Morgan's theorem.	6	L2	CO4
	d Prove the following expression using Boolean Identities. $A+BC = (A+B)(A+C)$	5	L3	CO4

OR

2	a Explain RC phase-shift oscillator with circuit diagram and necessary equations.	8	L2	CO3
	b What is a Flip-flop ? Explain the operation of master-slave JK flip-flop.	8	L2	CO4
	c Find i) $(398.75)_{10} = (?)_2$ ii) $(1011011110111110 . 11100011)_2 = (?)_{16}$	4	L3	CO4
	d Prove the following expression using Boolean Identities. $(A+B)(A'+C) = AC + A'B$	5	L3	CO4

PART B

3	a Explain the operation of IC-555 as an Astable oscillator	8	L2	CO3
---	--	---	----	-----

	with neat circuit diagram and necessary equations.	
b	With a block diagram explain the working of a 3-bit ripple counter.	6
c	Design full adder circuit and implement it using basic gates.	6
d	Implement the following function using NAND only. $F = A + CD' + D'E'$	5
OR		
4 a	With a neat circuit diagram explain the working of Wein-bridge oscillator.	8
b	What is multiplexer ? Implement 8:1 multiplexer using basic gates.	8
c	Perform the subtraction with the following binary numbers using 2's complements. i) 1010 - 0101 1100 - 1110	4
d	Implement the following function using NOR only. $F = (C' + A) (C' + E)$	5



Prepared by: Gurusandesh M 03/04/21